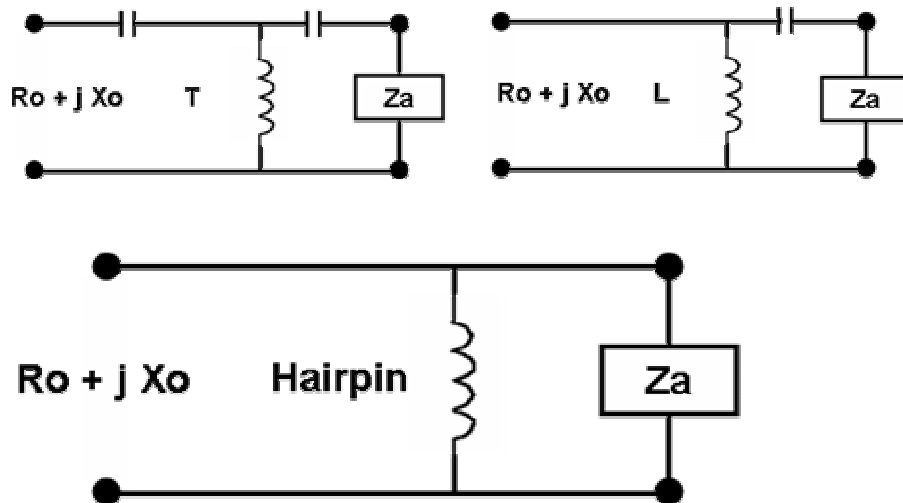


Subtleties of the Hairpin Matching

A number of matching networks have been employed such as the T, the L and the simplest the “Hairpin” as shown here.



For the T and L, the capacitor/inductors can be interchanged as needed, the hairpin is, by definition, just a single inductor. While the conventional configuration is indeed a single hairpin shaped loop, any inductor, such as a coil, is equally good from an electrical perspective. For lower frequency applications, a coil is pretty much required to get compact inductance.

The obvious beauty of the hairpin is simplicity since most of us have access to wire. The typical application for antennas is matching to a standard feedline impedance when the raw antenna shows moderate capacitive reactance and the resistive component is less than the desired feedline impedance.

Given a target feedline impedance of R_o , and a raw antenna impedance of $Z_a = R_a + jX_a$, X_a being negative, the condition to be met, if possible, in picking a shunt inductive reactance of X_L is

$$1/(R_o + j0) = 1/(jX_L) + 1/Z_a$$

for a perfect match. This perfect match is not generally possible for arbitrary Z_a and R_o . However, it is always possible to find an X_L that will yield an output impedance with a resistive component of R_o for any R_a . But this will be for only one value of X_a .

It is pretty easy to show that the requirement is

$$X_a = -[R_a(R_o - R_a)]^{1/2}$$


so then

$XL = -Z_a^2/X_a = -(R_a^2 + X_a^2)/X_a$ which uses the above X_a . This substitution provides

$$XL = (R_a^2 + R_a(R_o - R_a)) / [R_a(R_o - R_a)]^{1/2}$$


The plots of XL versus R_a in the ARRL Antenna Book (21st Ed, Figure 15 page 26-12) can be reproduced with this relation. You may note that the x-axis of that Antenna Book plot is mislabeled as Z_A - it should be the resistive component of Z_A that is called R_a here.

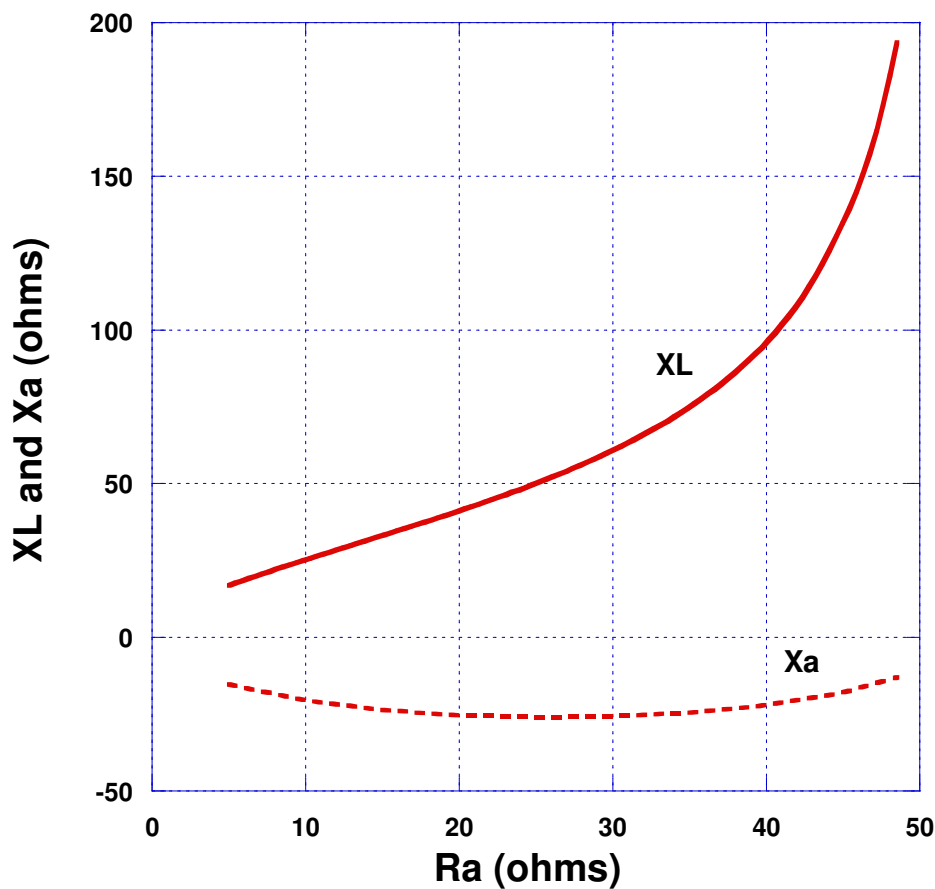Below is plot the results for the $R_o=52$ ohm case, along with the corresponding X_a value needed for a perfect match. Note that the value of X_a does not vary much and is ~ 20 ohms.




An alternate way of displaying the results that provides an indication of how close you need the X_a to be to its ideal value is to show as a contour plot the SWR available by the hairpin match for any (R_a, X_a) combination followed by the XL values that are required for this combination.

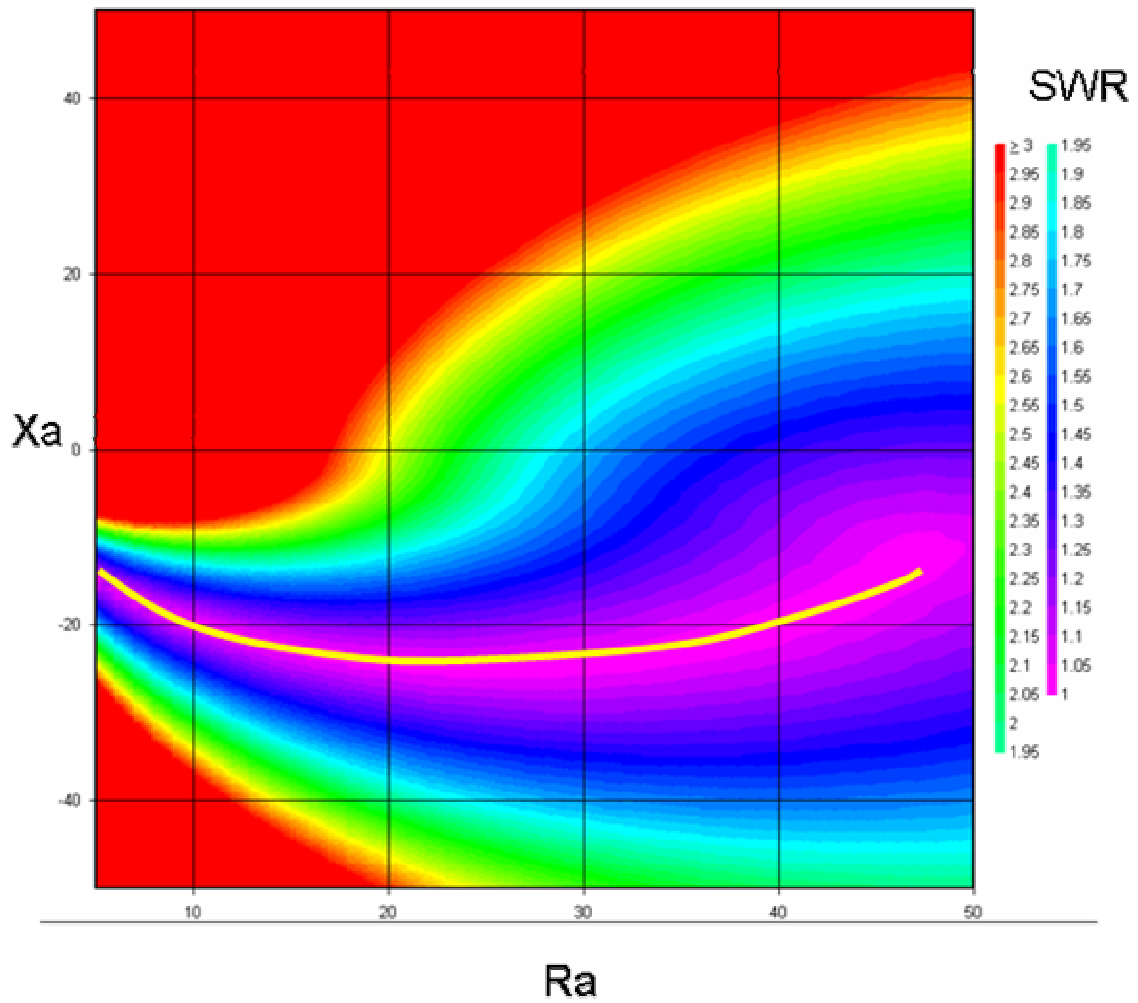A contour plot of SWR for the $Ro=50$ case over a wide range of Ra and Xa is given first. The yellow line shows approximately where an SWR of 1 is available.



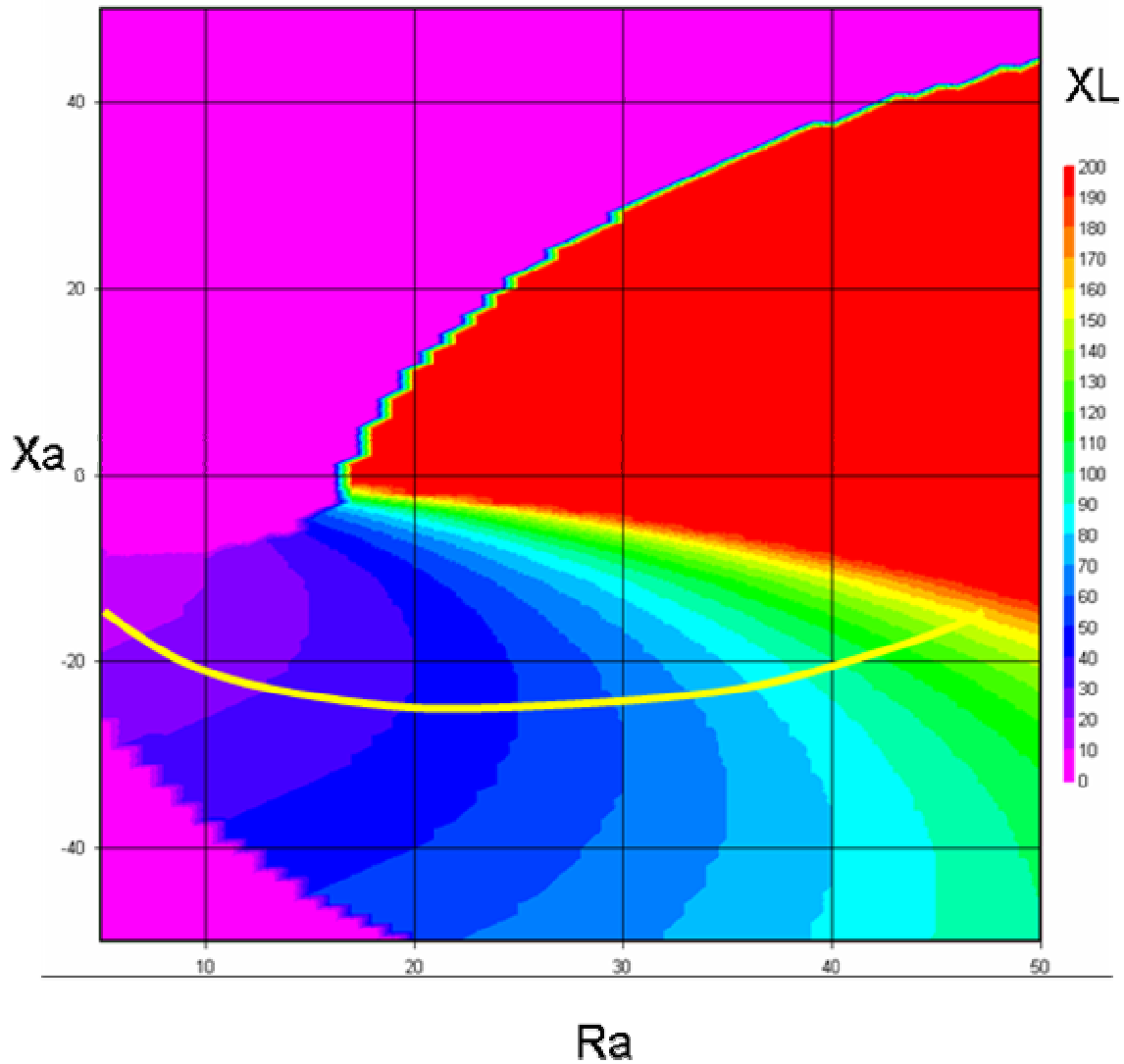The corresponding contour plot of XL for the same $Ro=50$ case is given next.



Given R_a and X_a , you might use the first contour plot to determine the best SWR available. The second plot would then indicate the needed XL . If you find that the SWR available is not acceptable, you may be able shorten or lengthen the antenna driven element to get a better pair of R_a and X_a values that will support a closer hairpin match.

It is left as a problem for the student to verify that the SWR has been correctly computed from R_o , R_a , X_a and XL .